

On the prototype the monostable was found to produce a 3.15-ms output quite reliably. In most applications where the servo is permanently built into the model, allowance for slight tolerances in pulsewidth can be made at the transmitter. However, if a pulse duration of exactly 3 ms is required, then C2 and C3 should be changed to 27 nF (0.027 μ F) and smaller capacitors connected in parallel until a pulse of exactly 3 ms is obtained on the oscilloscope. Even without a 'scope the pulsewidth can be accurately set by tweaking the value of C2 and C3 in the above fashion until the servo remains in exactly the neutral position with or without the polarity changer.

Practical aspects

The circuit is very simple to build from conventional parts on a single-sided circuit board (Figure 2). The actual build is shown in Figure 3, and a test setup with an Arduino as the servo pulse source, in Figure 4. The polarity changer consumes very little cur-

Component List

Resistors

R1,R2 = 10k Ω

Capacitors

C1 = 10 μ F 10V (preferably tantalum)
C2,C3 = 33nF

Semiconductors

IC1 = CD4001
D1 = 1N4148

Miscellaneous

K1,K2 = 3-pin pinheader, 0.1" pitch
PCB # 130340

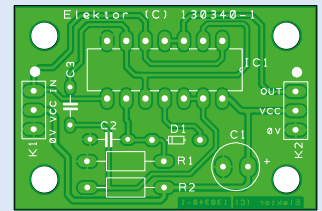


Figure 2. Printed circuit board design for the Servo Polarity Changer.

rent (1 mA), and is hardly affected (<2%) by variations in the supply voltage between 3 and 10 V. To keep the dimensions of the circuit to a minimum, a tantalum type is recommended for capacitor C1. As a result of the symmetrical configuration (R1 = R2; C2 = C3) the circuit has a low temperature coefficient.

(130340)

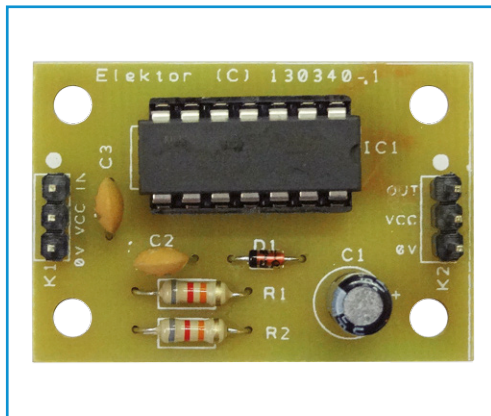


Figure 3. The finished board.

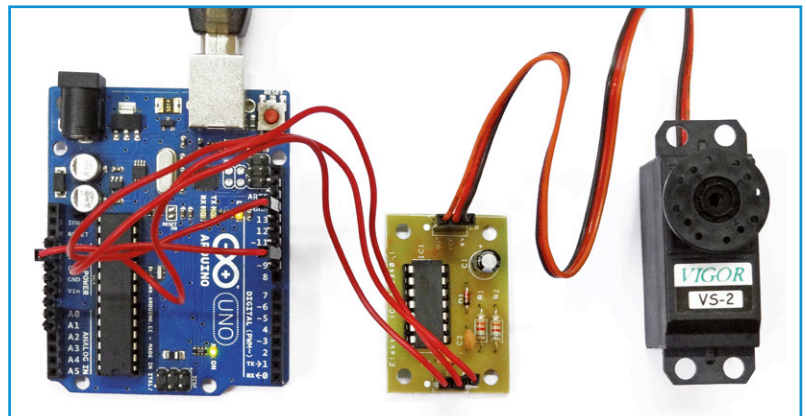


Figure 4. The operation of the circuit was verified using an Arduino microcomputer.