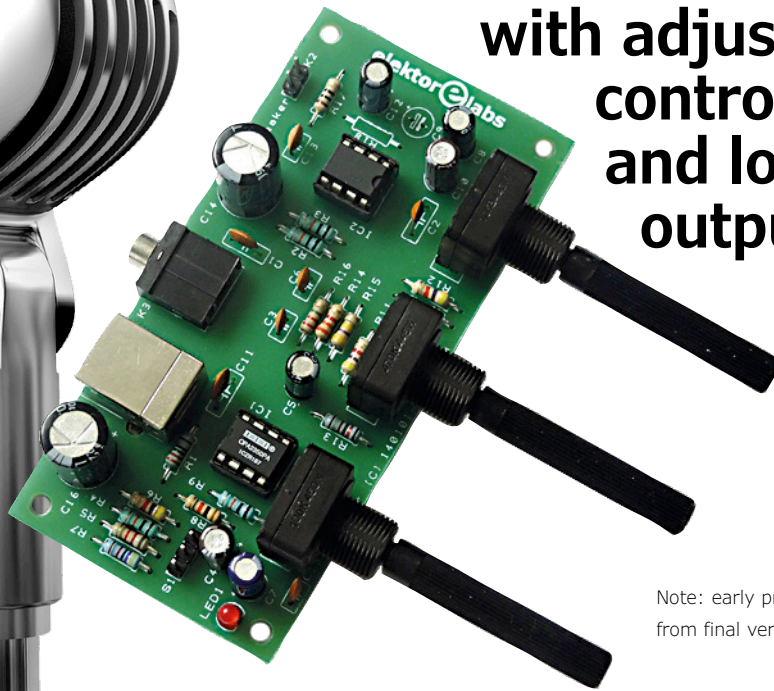




KaraOkay Microphone Amplifier

with adjustable tone control, USB power and loudspeaker output



By Elektor Labs India

Note: early prototype pictured; deviates in some respects from final version

Here is an all-analog, all-through-hole, cheap & cheerful preamplifier for that perennial problem of getting the microphone amplification just right, which is a challenge not only with the faithful reproduction of lead vocals during concerts and recordings, but also with campfire and karaoke-ish performances specially when the beer takes hold.

The two operational amplifiers of the circuit, IC1a and IC1b are contained in a single TLC272 package. The TLC272 was selected mainly for its low noise contribution, which is essential in a microphone (pre)amplifier as the original signal from the microphone is relatively weak (except for Matt Bel-


lamy on his Muse concerts). IC1a operates as a non-inverting amplifier with the electret microphone signal applied to pin 3 via coupling capacitor C1, and the bias voltage applied to the microphone element via R3. IC1a's amplification factor A is determined by the ratio of R8 to one of three combinations allowed by R4–R7. Let's call that resistance, R_{eq} . At switch position '1' i.e. with R5 switched into the circuit by S1, the factor will be:

$$R_{eq} = R4 \parallel R5 \parallel R7 = 449 \Omega$$

$$A_{(1)} = (1 + R8 / R_{eq}) = 223.7 \approx 47 \text{ dB}$$

Likewise with S1 at its center position a factor $A_{(2)}$ of about 14 (23 dB) is selected, and finally with R6 switched-in (S1 position 3) $A_{(3)}$ works out as 60 (35 dB). With selector S1 offering different gains, the circuit can be matched to different input levels, microphones, vocalists, and beer levels.

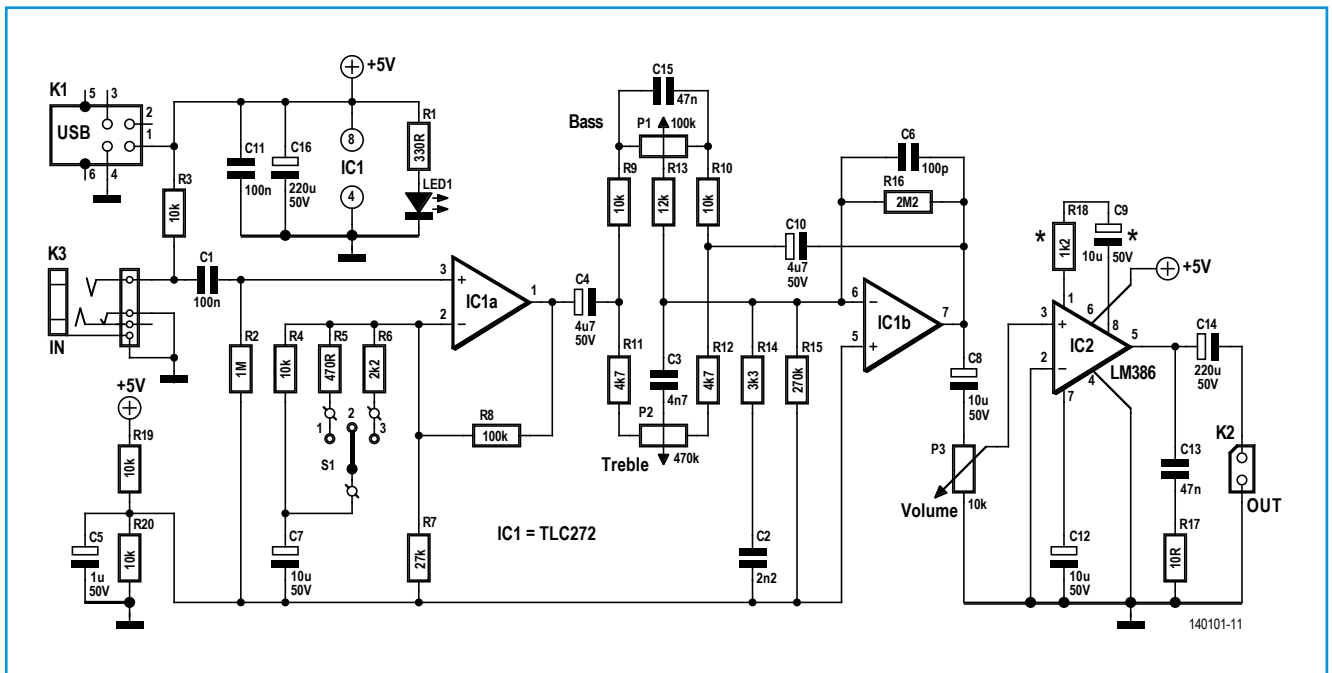The tone control stage is arranged around the next opamp, IC1b. Here the ratio R16/R15 sets the gain at about 18 dB. The effect of R14-C2 is, in principle, the same as R4





and C7: a smaller value of C2 increases the lower cutoff frequency. The real tone control however it the RC network inserted between IC1a and IC1b. Potentiometer P1 sets the bass level, and P2 the treble level. The two capacitors in the network, C15 and C3, behave as frequency-dependent resistances for alternating voltages.

The tone control stage is followed by a small power amplifier based on the venerable LM386 in standard configuration complete with Boucherot network C13-R17 to dampen out the effects of loudspeaker impedance fluctuations that may cause motorboating and other forms of instability.

Output power will be of the order of a few hundred milliwatts driving a small 8-ohm loudspeaker (kept well out of the microphone's vicinity). The LM386's gain is internally set to 20 to keep external part count low, but the addition of external parts R18-C9 between pins 1 and 8 allows the gain to be set to 20, 50 or 200. Without R18 and C9 the LM386's ampli-

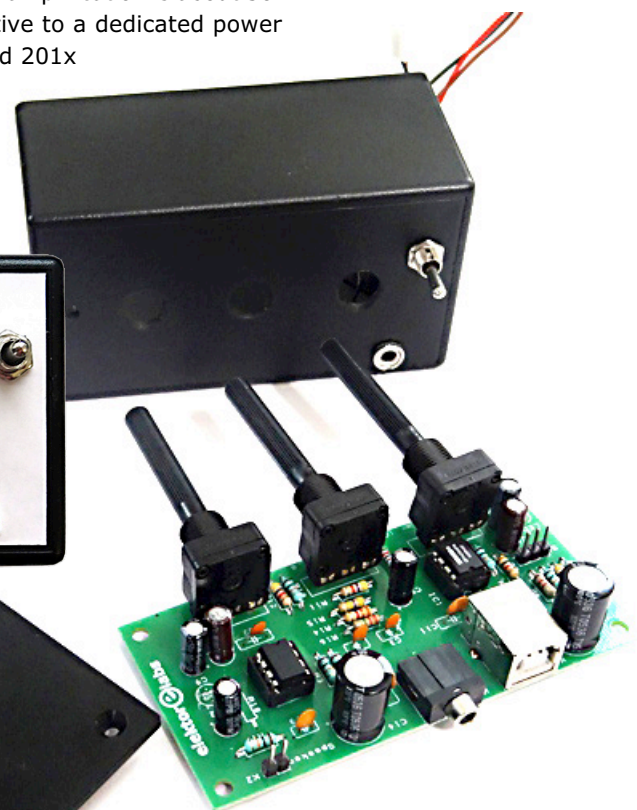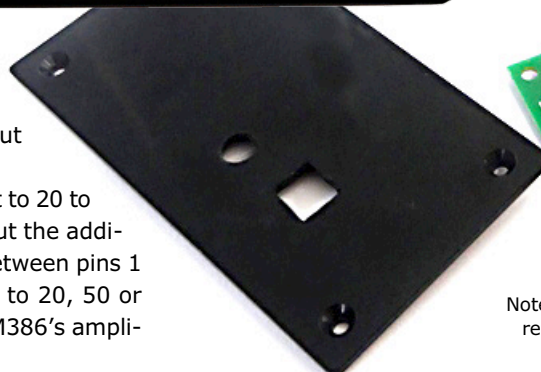fication is 20, which is recommended here. For an amplification of 200, fit capacitor C9 and replace R18 with a wire. With both R18 and C9 in place the amplification is about 50. As a good alternative to a dedicated power supply, and in good 201x fashion the amplifier is powered over a USB-B cable via K1, with interference sup-



Note: early prototype pictured; deviates in some respects from final version.

pression and some buffering afforded by C11 and C16 respectively.

The two opams are biased at 0.5 Vcc with the help of voltage divider R19-R20.

The circuit is built on the printed circuit board shown here, which was designed for compactness and low noise. The tone and volume controls P1, P2 and P3 as well as microphone

input and USB supply connectors K3 and K1 are all on the PCB, avoiding wiring that would make the circuit susceptible to hum and noise. The photos illustrate a suggested method of housing the amplifier board in a compact, strong but not beer resistant, ABS case.

(140101)

Component List

Resistors

- R1 = 330Ω
- R2 = 1MΩ
- R3,R4,R9,R10,R19,R20 = 10kΩ
- R5 = 470Ω
- R11,R12 = 4.7kΩ
- R6 = 2.2kΩ
- R7 = 27kΩ
- R8 = 100kΩ
- R13 = 12kΩ
- R14 = 3.3kΩ
- R15 = 270kΩ
- R16 = 2.2MΩ
- R17 = 10Ω
- R18 = 1.2kΩ (see text)
- P1 = 100kΩ lin. potentiometer
- P2 = 470kΩ lin. potentiometer
- P3 = 10kΩ log. potentiometer

Capacitors

- C1,C11 = 100nF 50V, X7R, 0.2" pitch
- C2 = 2.2nF 50V, 0.1" pitch
- C3 = 4.7nF 100V, X7R, 0.1" pitch
- C4,C10 = 4.7μF, 50 V, 2 mm pitch, 5x11 mm
- C5 = 1μF 50V, 2mm pitch

- C6 = 100pF 50V, Y5P, 0.1" pitch
- C7,C8,C9,C12 = 10μF 50V, 2mm pitch, 5x11 mm
- C13,C15 = 47nF 50V, X7R, 0.1" pitch
- C14,C16 = 220μF, 50V, 5mm pitch

Semiconductors

- IC1 = TLC272 or OPA2350PA
- IC2 = LM386
- LED1 = LED, red, 3mm

Miscellaneous

- K1 = USB type-B receptacle, right angle
- K2,S1 = SIL pinheader, 0.1" pitch
- K3 = 3.5-mm stereo jack socket, PCB mount
- S1 = switch, SPDT, center-off
- IC socket, DIP-8
- Casing, e.g. Bud Industries CU-793, Digikey # 377-1167-ND
- PCB # 140101

